

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ v_r \\ i_1 \\ i_r \end{bmatrix} =$$


$$\begin{bmatrix} -\frac{G_1 + G_r}{C_1} & \frac{G_r}{G_r} & -\frac{1}{L_1} & -\frac{1}{L_r} \\ 0 & 0 & 0 & 0 \end{bmatrix}$$



$$\begin{bmatrix} 0 & \frac{G_r}{G_1} & -\frac{1}{C_1} & -\frac{1}{C_r} \\ 0 & 0 & -\frac{1}{C_r} & -\frac{1}{C_1} \\ 0 & -\frac{G_r}{G_r} & 0 & 0 \\ -\frac{1}{L_r} & -\frac{1}{L_r} & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_r \\ i_1 \\ i_r \end{bmatrix}$$

$$+ \begin{bmatrix} -\frac{1}{C_1} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

I_s

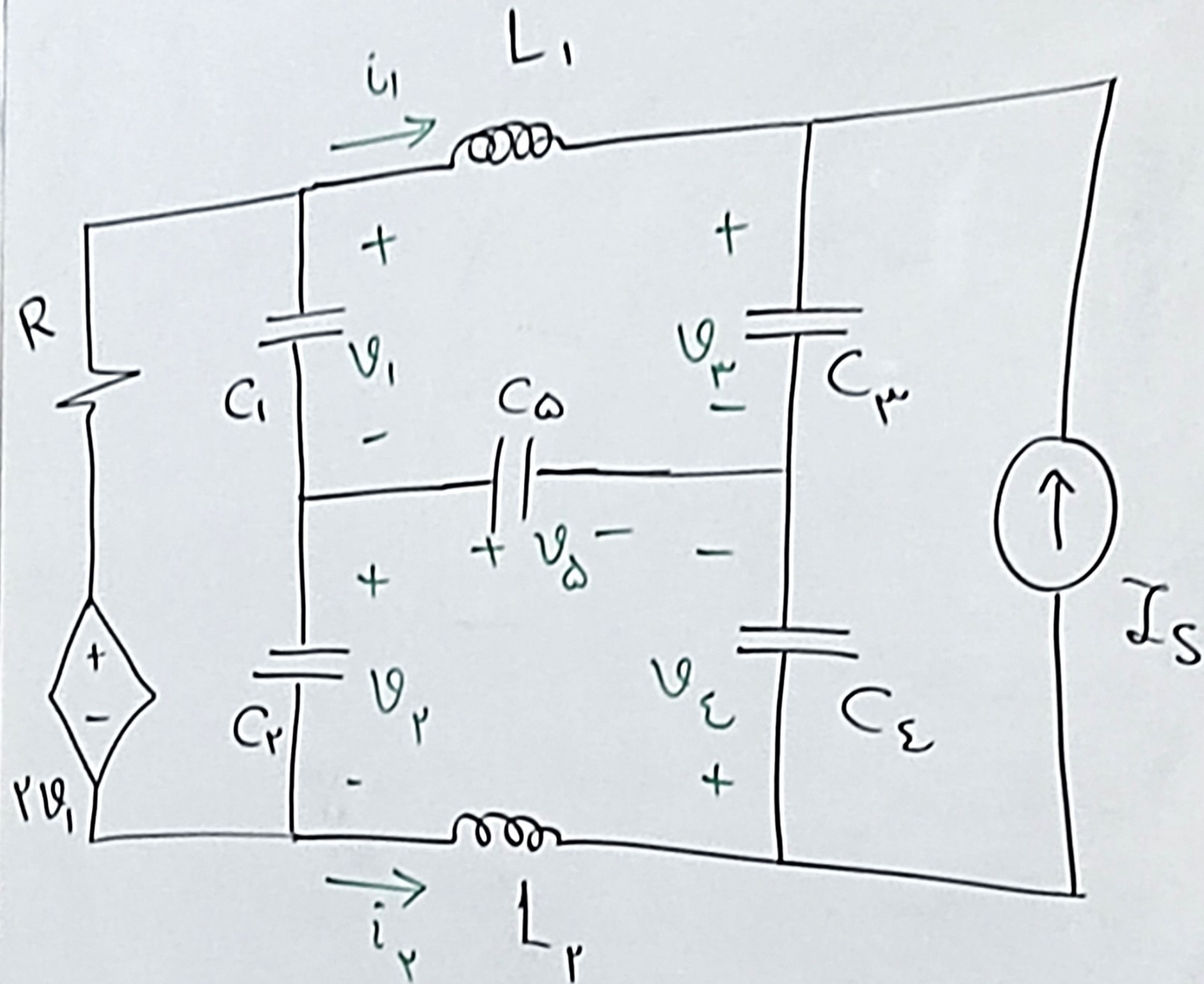

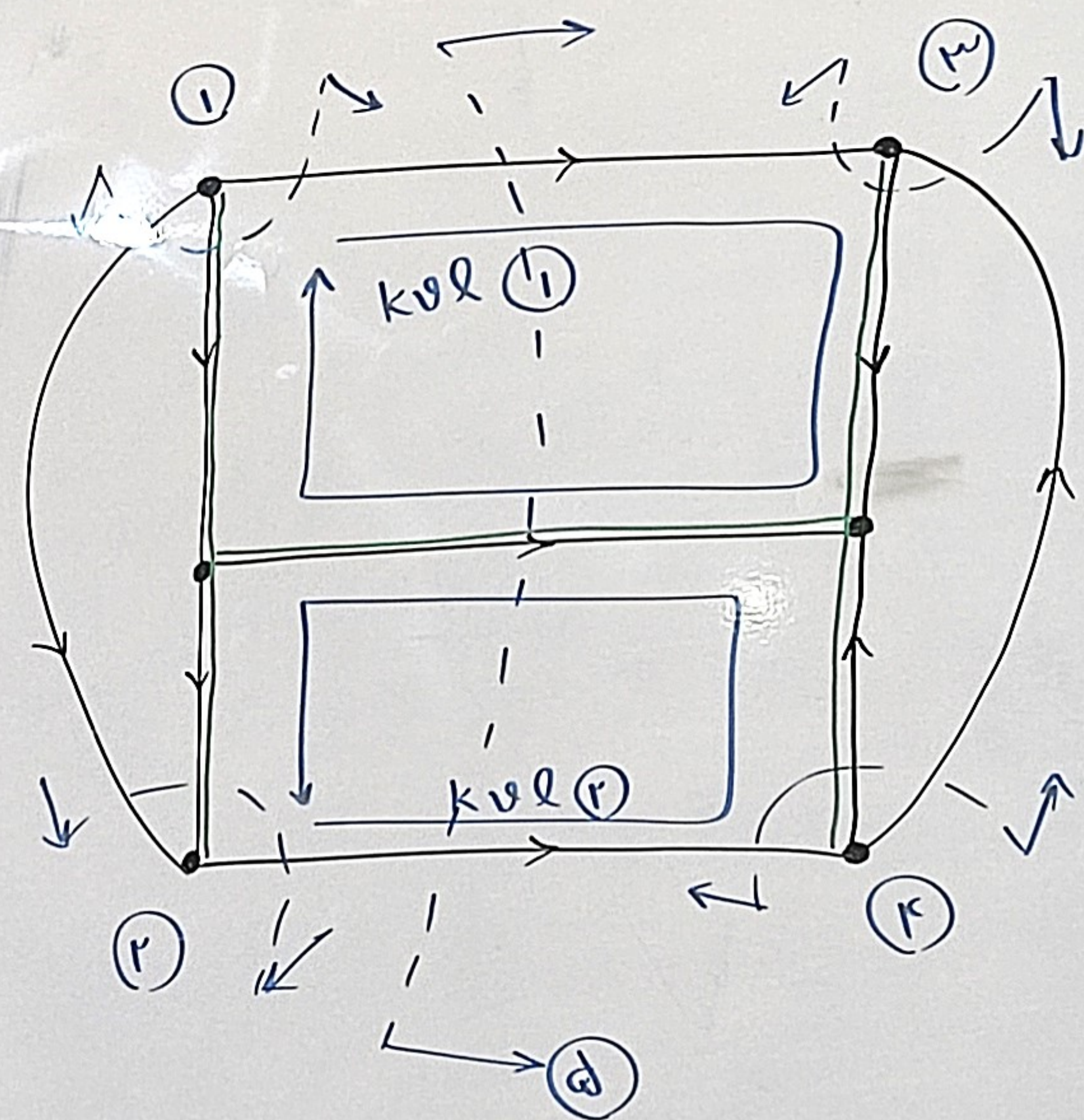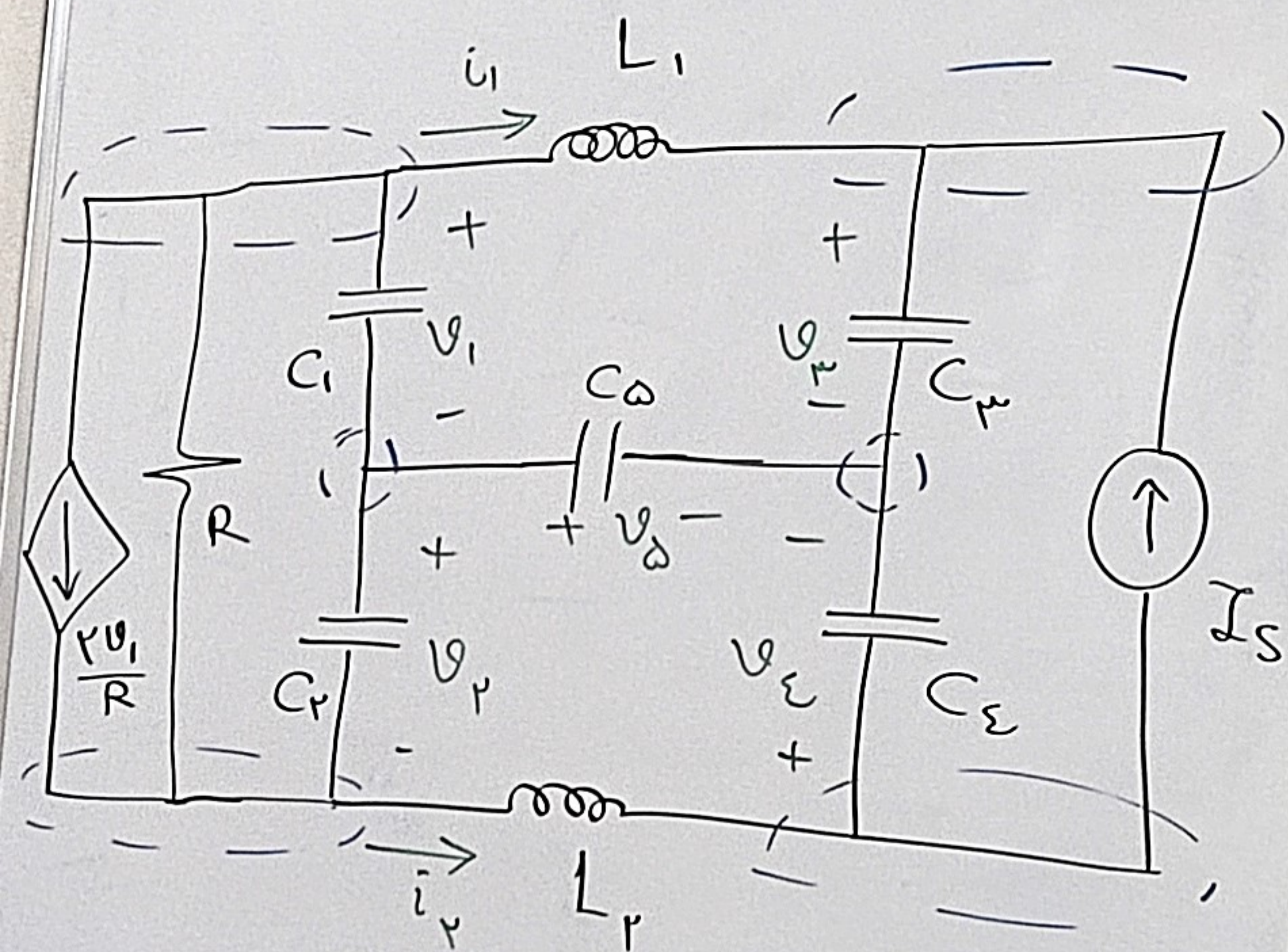




$$kcl(1) \left) \frac{v_1}{R} + \underbrace{I_R}_{\text{غير حالت}} + C_1 \frac{dv_1}{dt} + i_1 = 0 \quad (a)$$

$$kcl(2) \left) \frac{v_1}{R} + \underbrace{I_R}_{\text{غير حالت}} + C_r \frac{dv_r}{dt} - i_r = 0 \quad (b)$$

$$kcl(3) \left) C_r \frac{dv_r}{dt} - i_1 - I_s = 0$$

$$\frac{dv_r}{dt} = \frac{1}{C_r} i_1 + \frac{1}{C_r} I_s \quad (c)$$
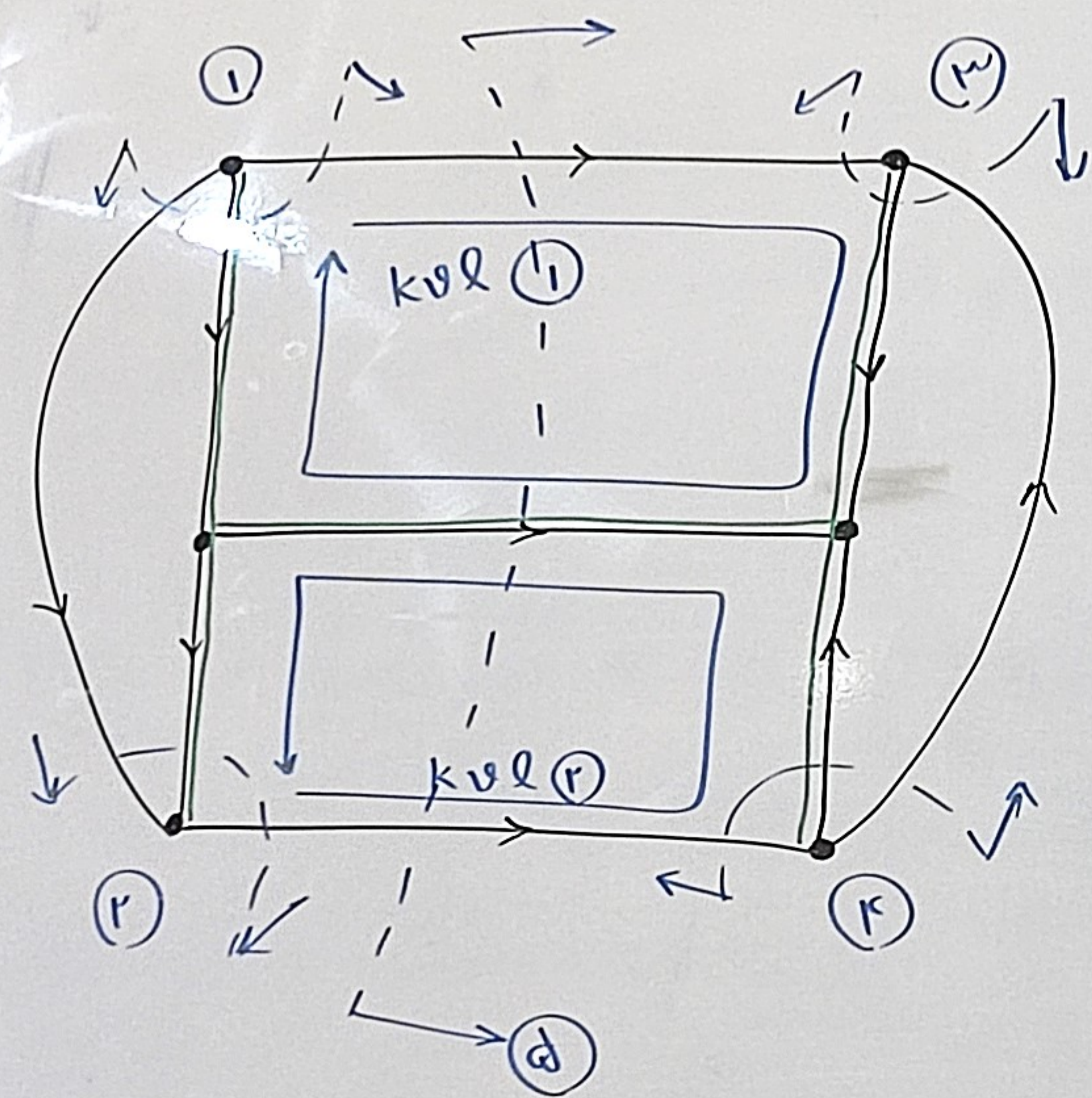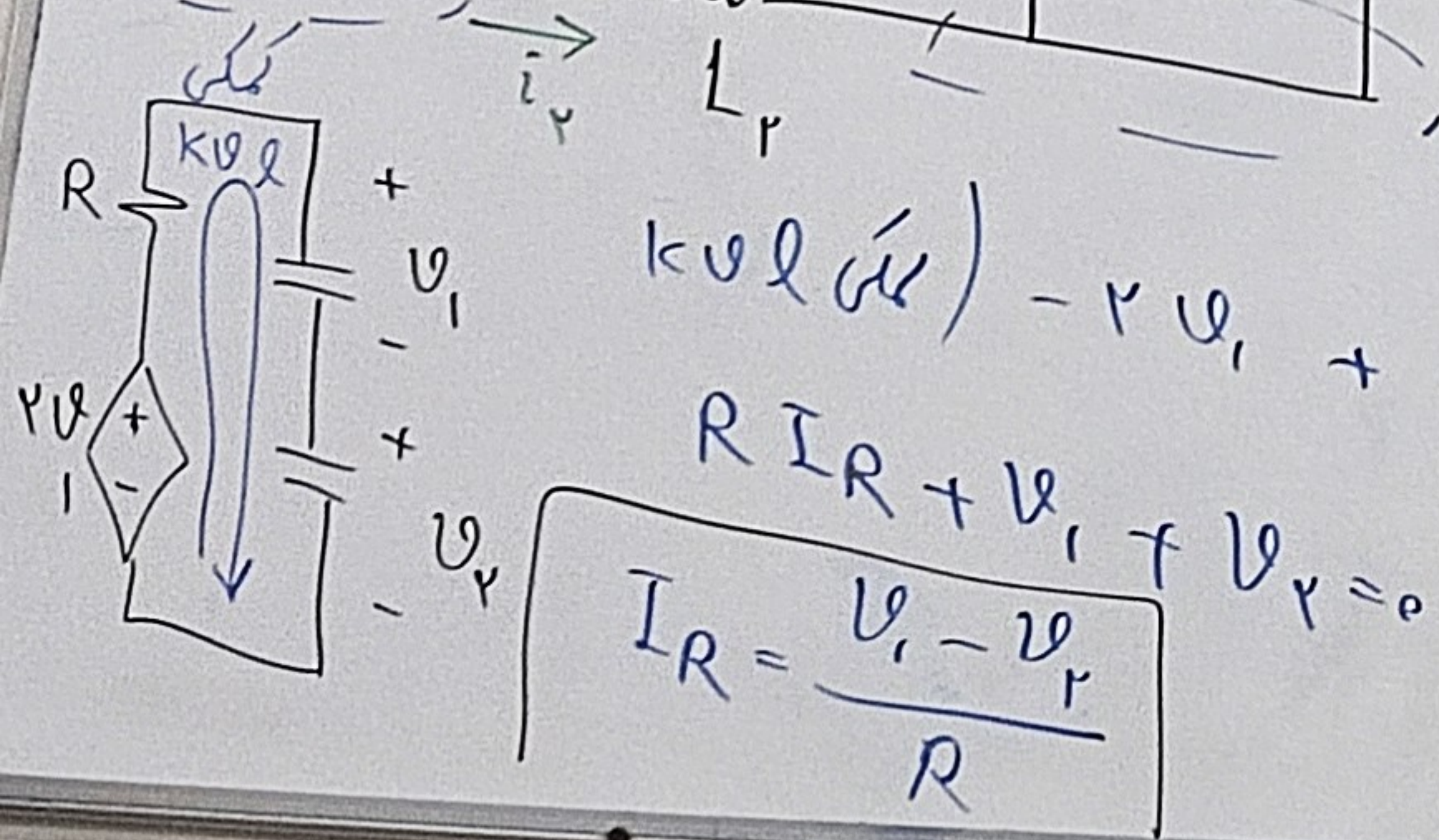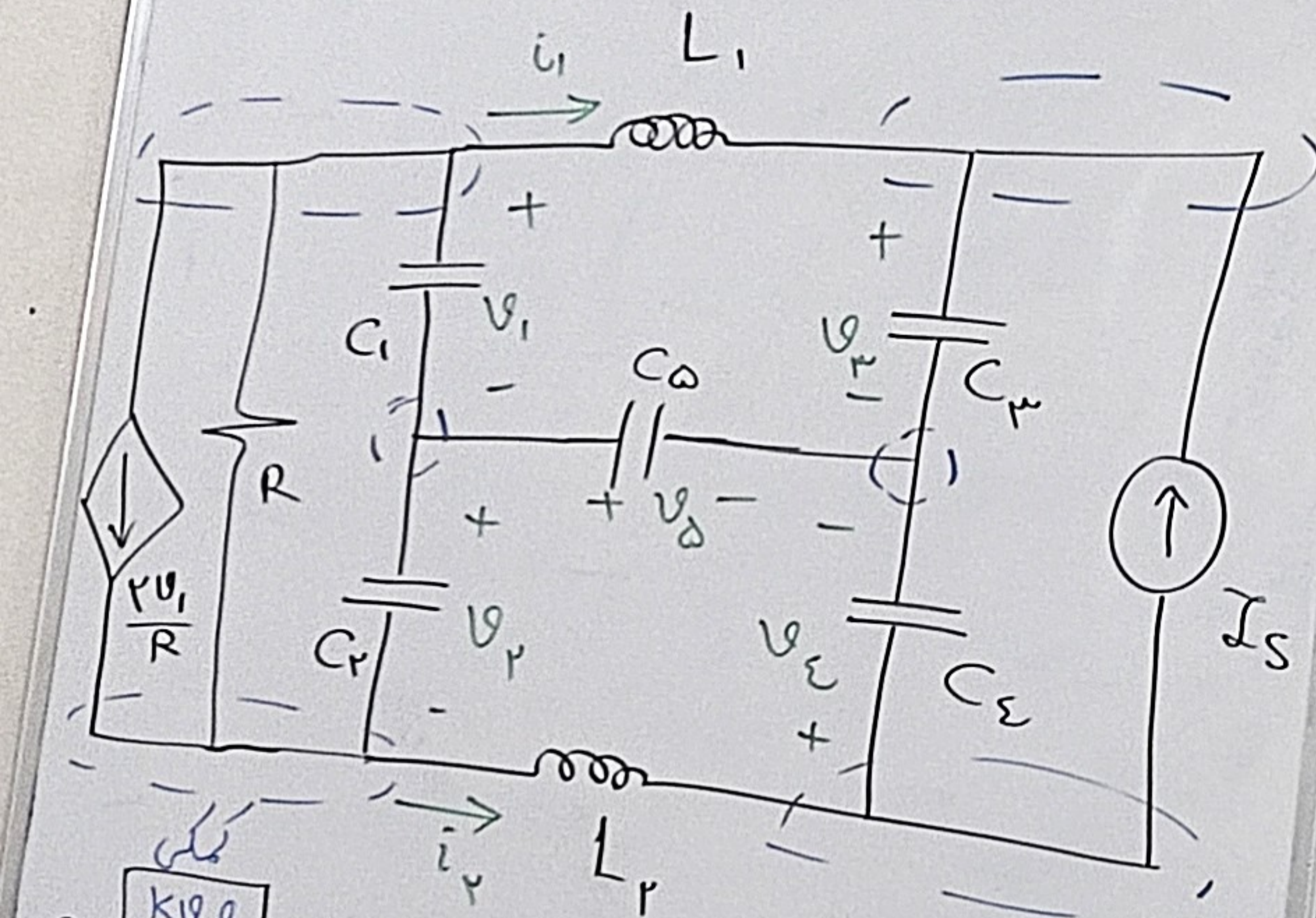
$$kcl(4) \left) -i_r + C_\varepsilon \frac{dv_\varepsilon}{dt} + I_s = 0 \Rightarrow \frac{dv_\varepsilon}{dt} = \frac{1}{C_\varepsilon} i_r - \frac{1}{C_\varepsilon} I_s \quad (d)$$



$$kvl(1) \quad L_1 \frac{di_1}{dt} + v_r - v_0 - v_1 = 0$$

$$kvl(2) \quad L_r \frac{di_r}{dt} + v_0 + v_r - v_0 + v_r = 0 \Rightarrow \frac{di_r}{dt} = -\frac{1}{L_r} v_r - \frac{1}{L_r} v_0 + \frac{1}{L_r} v_0$$



$$kcl(1) \quad \frac{v_1}{R} + I_R + C_1 \frac{dv_1}{dt} + i_1 = 0$$

$$kcl(2) \quad \frac{v_1}{R} + I_R + C_r \frac{dv_r}{dt} - i_r = 0$$

$$kvl(1) \quad L_1 \frac{di_1}{dt} + v_r - v_0 - v_1 = 0$$

$$\frac{di_1}{dt} = \frac{1}{L_1} v_1 - \frac{1}{L_1} v_r + \frac{1}{L_1} v_0$$
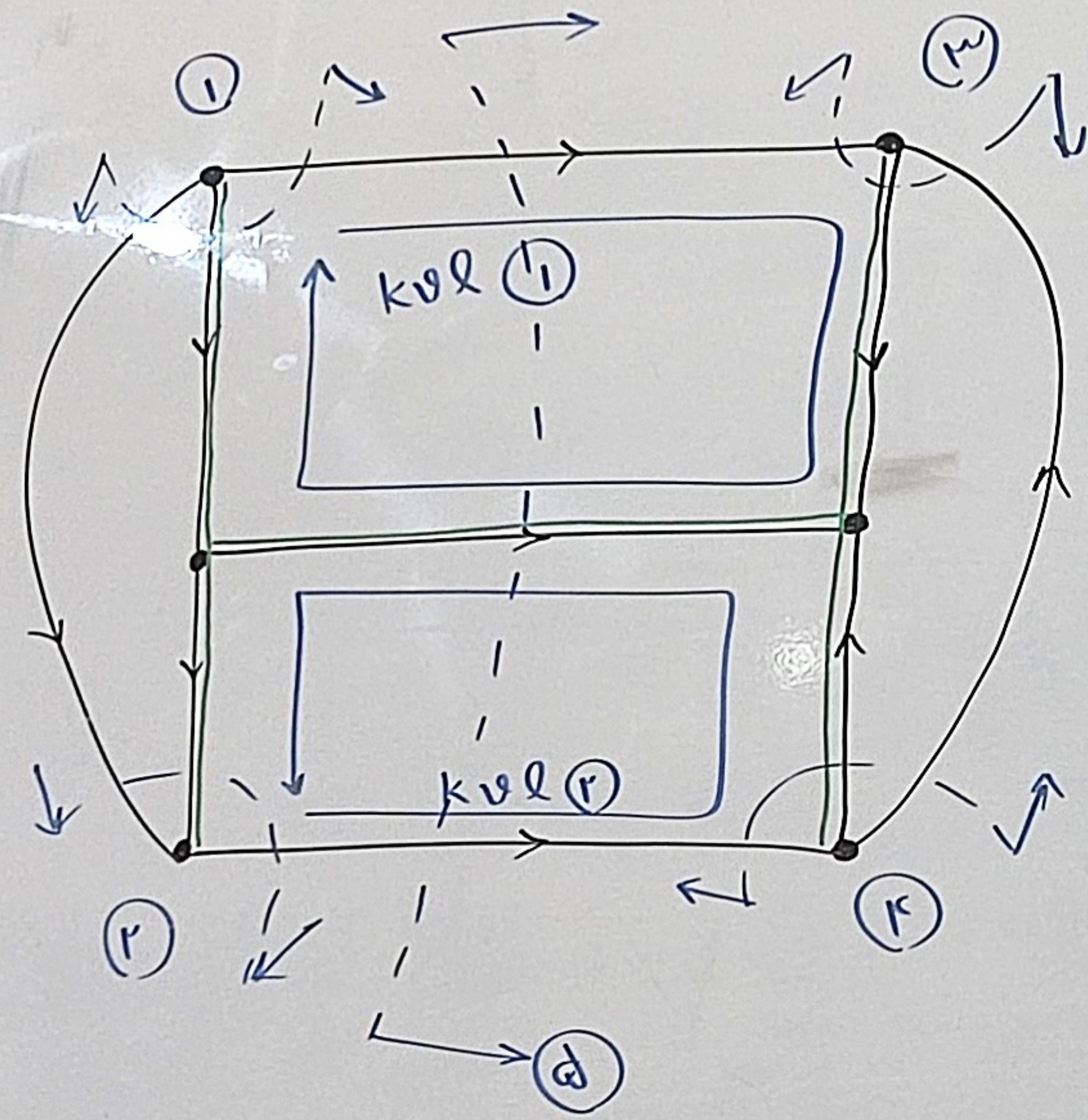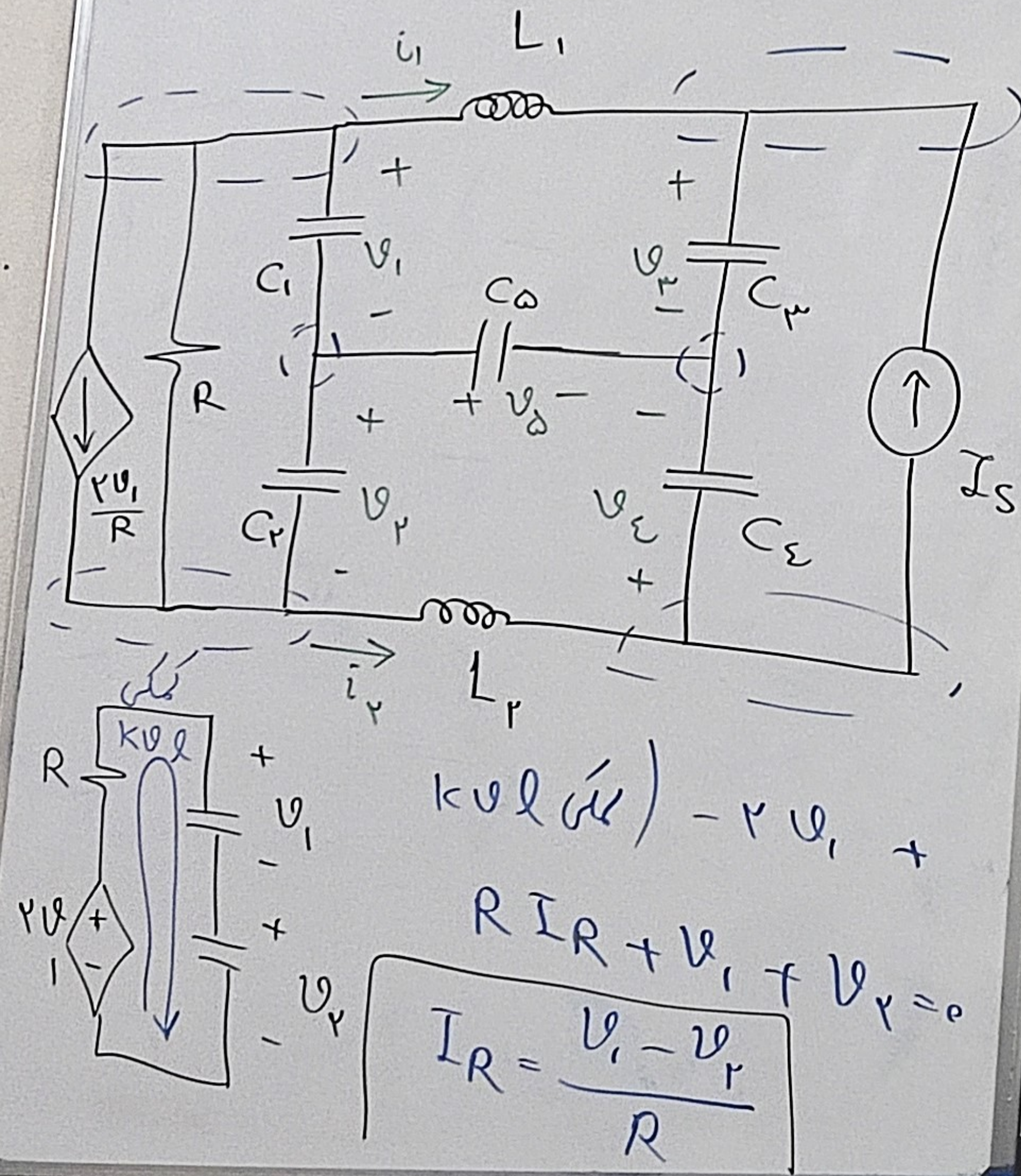
$$\frac{di_r}{dt} = -\frac{1}{L_r} v_r - \frac{1}{L_r} v_0 + \frac{1}{L_r} v_0$$



$$KVL(1) \quad L_r \frac{di_r}{dt} + v_\varepsilon - v_d + v_r = 0 \Rightarrow \frac{di_r}{dt} = -\frac{1}{L_r} v_r - \frac{1}{L_r} v_\varepsilon + \frac{1}{L_r} v_d$$

$$KCL(1) \quad \frac{v_1}{R} + I_R + C_1 \frac{dv_1}{dt} + i_1 = 0$$

$$KCL(2) \quad \frac{v_1}{R} + I_R + C_r \frac{dv_r}{dt} - i_r = 0$$

$$KCL(3) \quad C_d \frac{dv_d}{dt} + i_1 + i_r = 0$$

$$\frac{dv_d}{dt} = -\frac{1}{C_d} i_1 - \frac{1}{C_d} i_r$$

جائیداری معادله می شود $\Rightarrow$

ب) $\sim \sim \sim \Rightarrow$

$$I_R = \frac{V_i - V_r}{R}$$

$$\frac{V_i}{R} + \frac{V_i - V_r}{R} + C_1 \frac{dV_i}{dt} + i_1 = 0 \Rightarrow \frac{dV_i}{dt} = \frac{-3}{RC_1} V_i + \frac{1}{RC_1} V_r - \frac{1}{C_1} i_1 \quad (1)$$

$$\frac{V_i}{R} + \frac{V_i - V_r}{R} + C_r \frac{dV_r}{dt} - i_r = 0 \Rightarrow \frac{dV_r}{dt} = \frac{-3}{RC_r} V_i + \frac{1}{RC_r} V_r + \frac{1}{C_r} i_r \quad (2)$$

$\frac{d}{dt}$

$$\begin{bmatrix} \dot{v}_1 \\ \dot{v}_r \\ \dot{v}_e \\ \dot{v}_a \\ \dot{i}_1 \\ \dot{i}_r \end{bmatrix} = \begin{bmatrix} -\frac{r}{RC_1} & \frac{1}{RC_1} \\ -\frac{r}{RC_1} & \frac{1}{RC_1} \\ 0 & 0 \\ 0 & 0 \\ -\frac{1}{L_1} & 0 \\ 0 & -\frac{1}{L_r} \end{bmatrix} \begin{bmatrix} v_1 \\ v_r \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & 0 & 0 & -\frac{1}{C_1} & 0 \\ 0 & 0 & 0 & 0 & -\frac{1}{C_r} \\ 0 & 0 & 0 & -\frac{1}{C_r} & 0 \\ 0 & 0 & 0 & 0 & -\frac{1}{C_2} \\ 0 & 0 & -\frac{1}{C_2} & -\frac{1}{C_3} & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_r \\ v_e \\ v_a \\ i_1 \\ i_r \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ -\frac{1}{C_r} \\ -\frac{1}{C_3} \\ 0 \\ 0 \end{bmatrix} I_s$$

$D = S = j\omega$

